

P02 Latex


arif.mammadov

March 2018

# Chapter 1
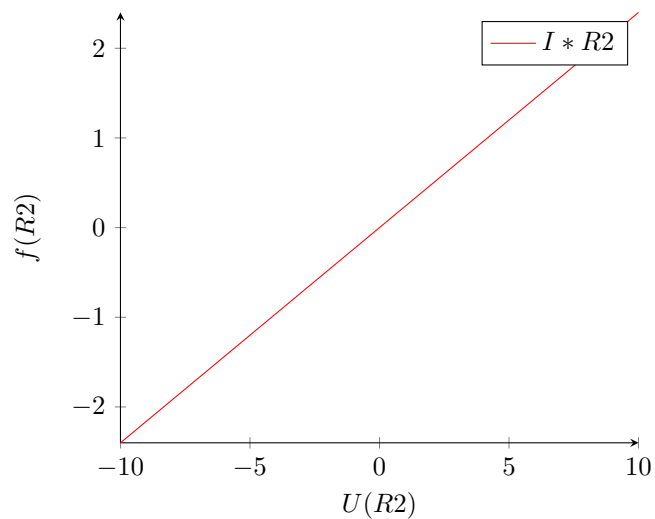
## Theoretical part

[scale=1.2, every node/.style=transform shape] (0,0) to[battery= $V$ ] (0,4)  
to[resistor= $R1$ ] (6,4) to[resistor= $R2$ ] (6,0) – (0,0) ;



### 1.1 Circuit calculation

R1	2
R2	3
V1	1.2
$U_{R1}$	0.48
$U_{R2}$	0.72

## Chapter 2

# Practical part

### 2.1 Work with GEDA programs


#### 2.1.1 Work with gschem[?]


In this section we opened Gschem program with help of command "gschem". Then we created the circuit based on digits on our ID

#### 2.1.2 Work with gnetlist
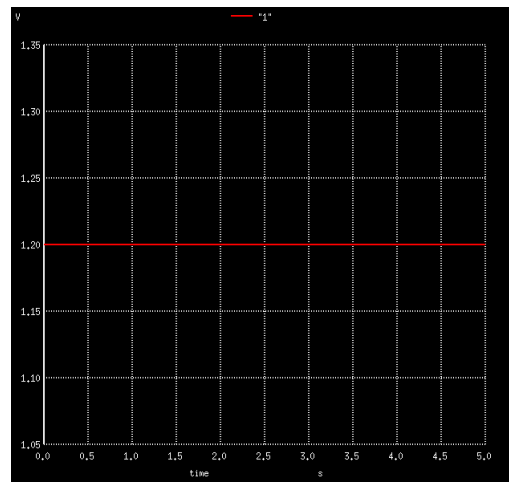
#### 2.1.3 Work with ngspice[?]

With the help of ngspice we declared time to see our values in a graphical form. Then we got our graphs by the function "plot".



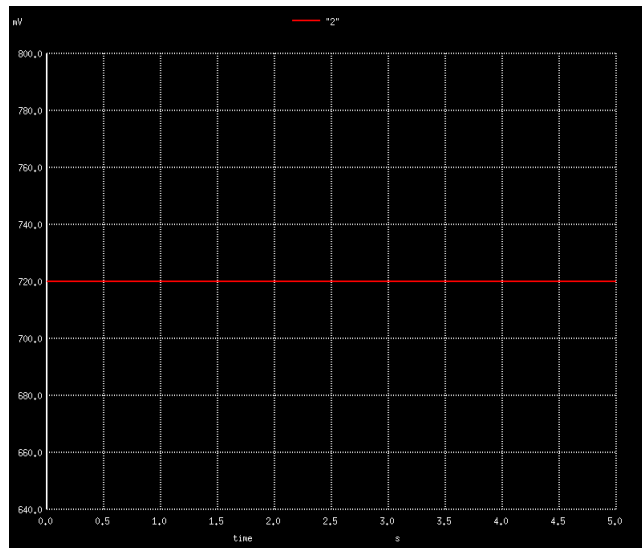

## 2.2 work with QUCS programs

Since it was optional to do this part, I have skipped this section.

# Bibliography

- [1] The program for drawing circuits
- [2] The program for plotting functions and circuits